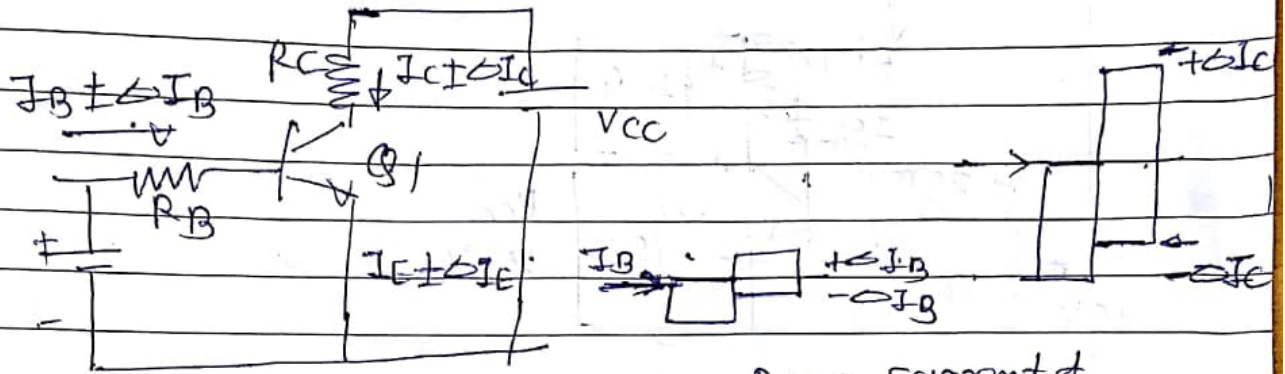


## Current Amplification



Current levels & current changes

Base current & collector currents

A small change in base current ( $\Delta I_B$ ) produces a large change in collector current ( $\Delta I_C$ ) and a large change in emitter current ( $\Delta I_E$ ).

$$\beta_{dc} = \frac{\Delta I_C}{\Delta I_B}$$

The increasing & decreasing levels of input & output currents may be defined as alternating quantities. In this case, small letters are used for the subscripts. Thus  $i_b$  is an ac base current,  $i_c$  is an ac collector current &  $i_e$  is an ac emitter current.


The alternating current gain from base to collector may is

$$\beta_{ac} = \frac{i_c}{i_b} \quad \left( \beta_{dc} \text{ or } h_{fe} \right)$$

for common emitter  
circuit,

given in  
data  
sheets.

## Voltage Amplification.

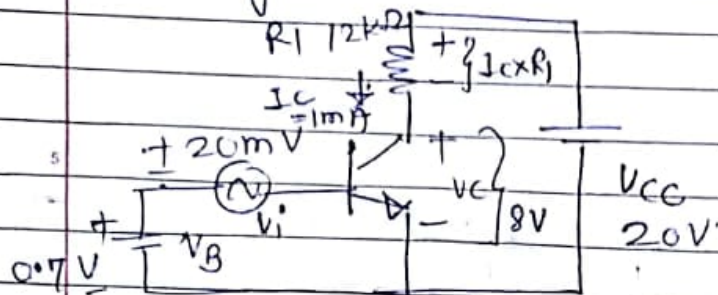

here  $V_B$  is 0.7 V to forward bias base emitter junction. It produces 20  $\mu$ A base current. This gives

$$I_C = \beta_{DC} I_B = 50 \times 20 \mu A$$

$$I_C = 1 \text{ mA}$$

dc level of transistor collector voltage is  $V_C = V_{CC} - (I_C R_1)$

$$= 20 - (1 \times 10^{-3} \times 12 \times 10^3)$$

$$V_C = 8 \text{ V} \quad \text{shown in fig}$$

ac  $I_P$  voltage is zero  $V_C$  is 8 V.

Now  $V_i$  causes base voltage variation, ( $\Delta V_B$ ) of  $\pm 20 \text{ mV}$ , then base current changes by  $\pm 5 \mu A$  (Assume) This change produces change in the collector current

$$\Delta I_C = \beta_{DC} \Delta I_B = 50 (\pm 5 \mu A)$$

$$\Delta I_C = \pm 250 \mu A$$

This  $\Delta I_C$  causes change in V.D across  $R_1$ .

$$\Delta V_C = \Delta I_C R_1 = \pm 250 \mu A \times 12 \text{ k}\Omega$$

$$\Delta V_C = \pm 3 \text{ V}$$

Now  $A_v = \frac{\Delta V_c}{\Delta V_B} = \frac{\pm 3V}{\pm 20mV}$


$= 150$

Small ac  $\pi$ P base voltage change ( $\Delta V_B$ ) <sup>( $\pm 20mV$ )</sup>  
causes a large ac o/p change ( $\Delta V_c$ )  
to  $(\pm 3V)$

Here we get voltage gain (amplification factor) of 150



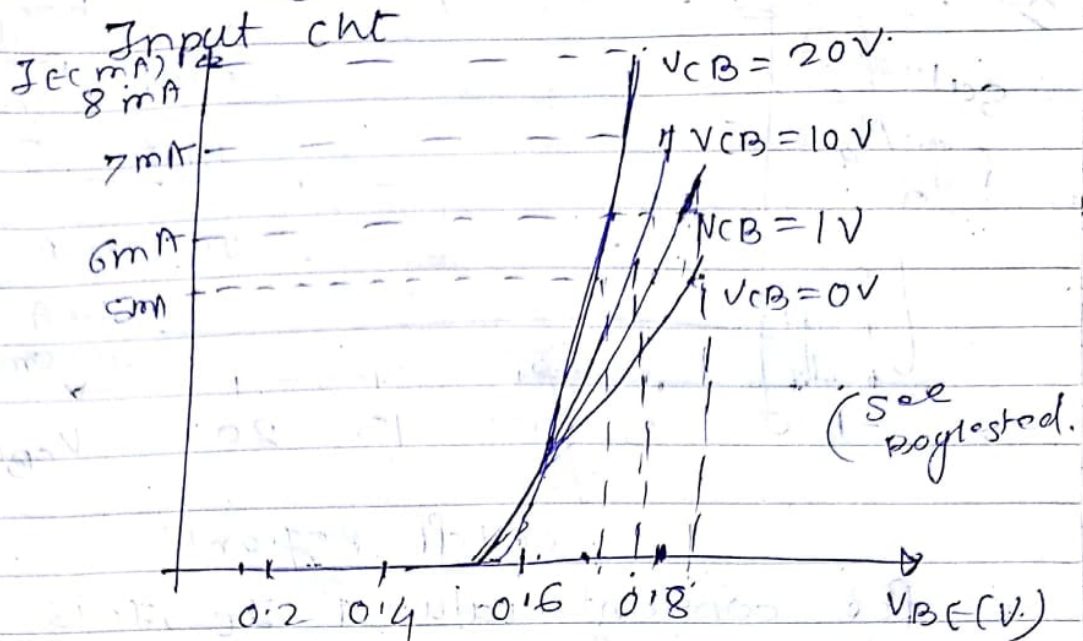To get the same value of  $I_E$  as that of for  $V_{CB}=0$ , you need to decrease  $V_{BE}$  hence curve shifts to left  
CB config I/P chrt.



Input or driving pt chrt for a CB for si transistor amp<sup>r</sup>

\* When  $V_{CB}$  is equal to 0, emitter base junction is forward biased, junction behaves as diode,  $I_E$  & rapidly with small increase in  $V_{BE}$ .


\* Base width reduces which shortens the distance & reduces the resistance b/w emitter & base and collector base depletion region. When  $V_{CB}$  is increased keeping  $V_{BE}$  constant the width of base region decreases. This results in increase in  $I_E$ . Therefore curve shifts toward left as  $V_{CB}$  ↑.

(To get same  $I_E$  as that of  $V_{CB}=0$ ,  $V_{BE}$  ↓.)  
 \* see previous chrt scratched one  
output characteristics

\* Here  $I_E$  is kept constant by adjusting  $V_{BE}$ . Then  $V_{CB}$ 's & in suitable equal steps and the collector current  $I_C$  is noted for each value of  $I_E$ . This is repeated for different fixed values of  $I_E$ .



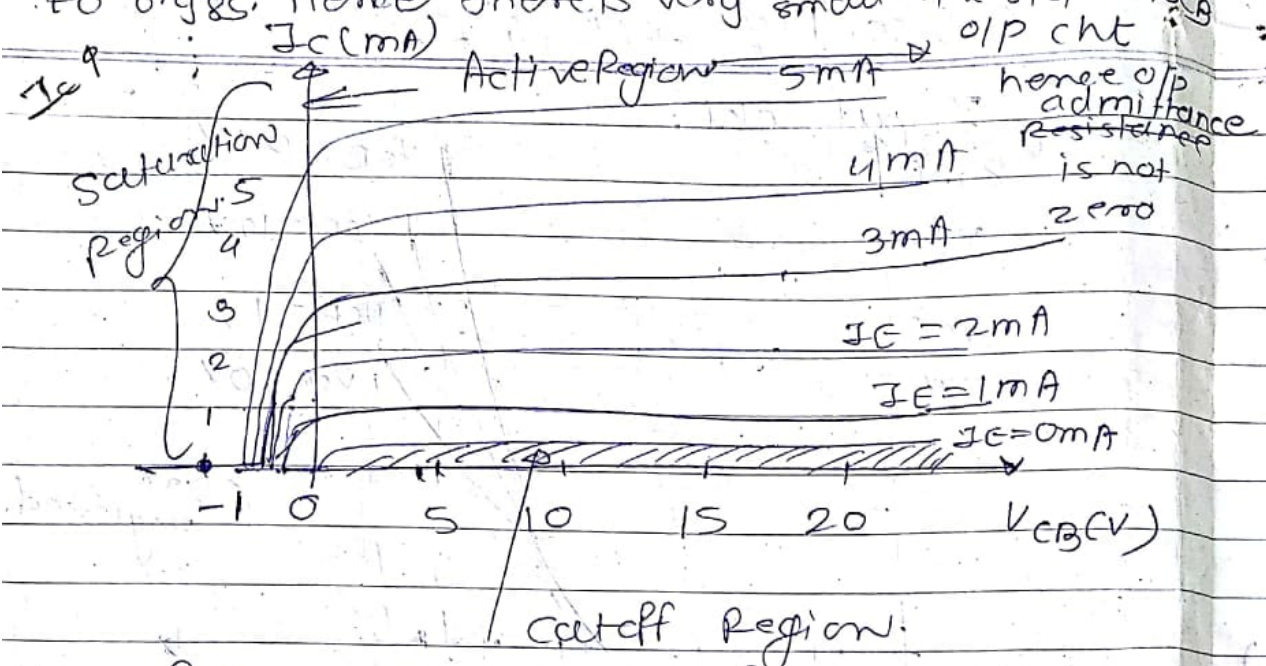\* For higher values of  $V_{CB}$  due to Early effect the value of  $\alpha$  increases, say  $\alpha$  changes from 0.98 to 0.995. Hence there is very small +ve slope in  $I_C$  o/p chrt.



For constant value of  $I_E$ ,  $I_C$  is independent of  $V_{CB}$  and curves are parallel to x axis.

\*

even when  $V_{CB} = 0$ , BE junction is forward biased, majority charge carriers  $\bar{e}$  crosses the barrier (depletion region) at CB junction and gives rise to  $I_C$ .

Saturation

Active Region = BE + CB Forward Biased

Cutoff region = BE and CB both Reverse biased,

Active Region = BE j<sup>n</sup> FB + BC j<sup>n</sup> Reverse biased

In the cutoff region (or lower end of active region),  $I_E$  is zero, the collector current is simply due to reverse saturation collector leakage current  $I_{CBO}$ . It is microamperes.

The slope of CB ckt will give following ckt. Since these parameter have different dimensions, they are commonly called h (hybrid) Parameters.

① Input Impedance ( $h_{ib}$ )

$$h_{ib} = \frac{\Delta V_{EB}}{\Delta I_E} \quad \left| \begin{array}{l} V_{CB} \text{ constant} \end{array} \right.$$

typical value ranges from  $20\Omega$  to  $50\Omega$ .  
This is calculated from CB ZIP ckt

② Gain

Forward Current gain ( $h_{fb}$ )

$$h_{fb} = \frac{\Delta I_C}{\Delta I_E} \quad \left| \begin{array}{l} V_{CB} \text{ constant} \end{array} \right.$$

typical value 0.9 to 1.0.

This slope of  $I_C$  versus  $I_E$  curve (o/p ckt)

③ o/p Impedance admittance

$$h_{ob} = \frac{\Delta I_C}{\Delta V_{CB}} \quad \left| \begin{array}{l} I_E \text{ constant} \end{array} \right.$$

This is slope of  $I_C$  versus  $V_{CB}$  from o/p ckt

Typical value is 0.1 to  $10\mu\text{mhos}$

or o/p Resistance is high  
typical value  $1\text{M}\Omega$

④ Reverse voltage gain

$$h_{rb} = \frac{\Delta V_{EB}}{\Delta V_{CB}} \quad \left| \begin{array}{l} I_E \text{ constant} \end{array} \right.$$


slope of  $V_{EB}$  vs  $V_{CB}$ , from ZIP ckt  
Typical value  $10^{-5}$  to  $10^{-4}$


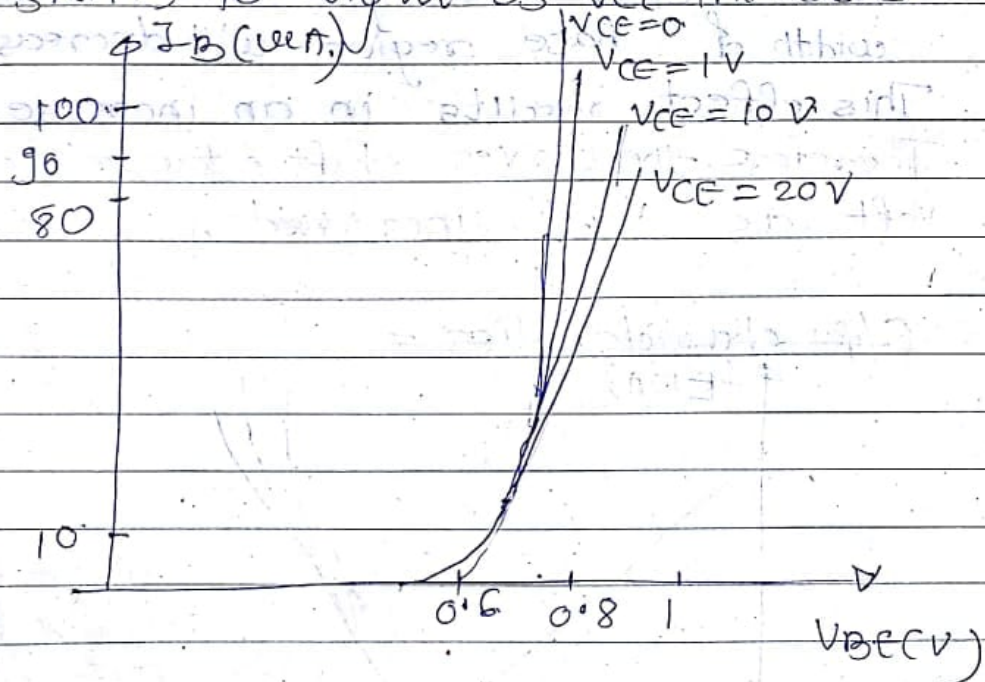
## CE configuration


3/1 P. ch. 1 -  $V_{CE}$  is kept constant  
Say  $V_{CE} = 0V$ , then  $I_B$  is plotted by increasing  $V_{BE}$  in equal steps.  
Then  $V_{CE}$  is ~~repeated~~ changed and procedure is repeated.

At  $V_{CE} = 0$  EBJ is forward biased & behaves like a diode & hence we get  $I_B$ .  
Now when  $V_{CE}$  is increased, the width of depletion region goes on increasing hence effective width of Base decreases. Hence less recombination of holes & electrons take place and ~~effectively~~  $I_B \downarrow$ . (hence to get the same value of  $I_B$  as that for  $V_{CE} = 0$ ,  $V_{BE}$  should be increased.) Therefore curve shifts to right as  $V_{CE}$  increases.


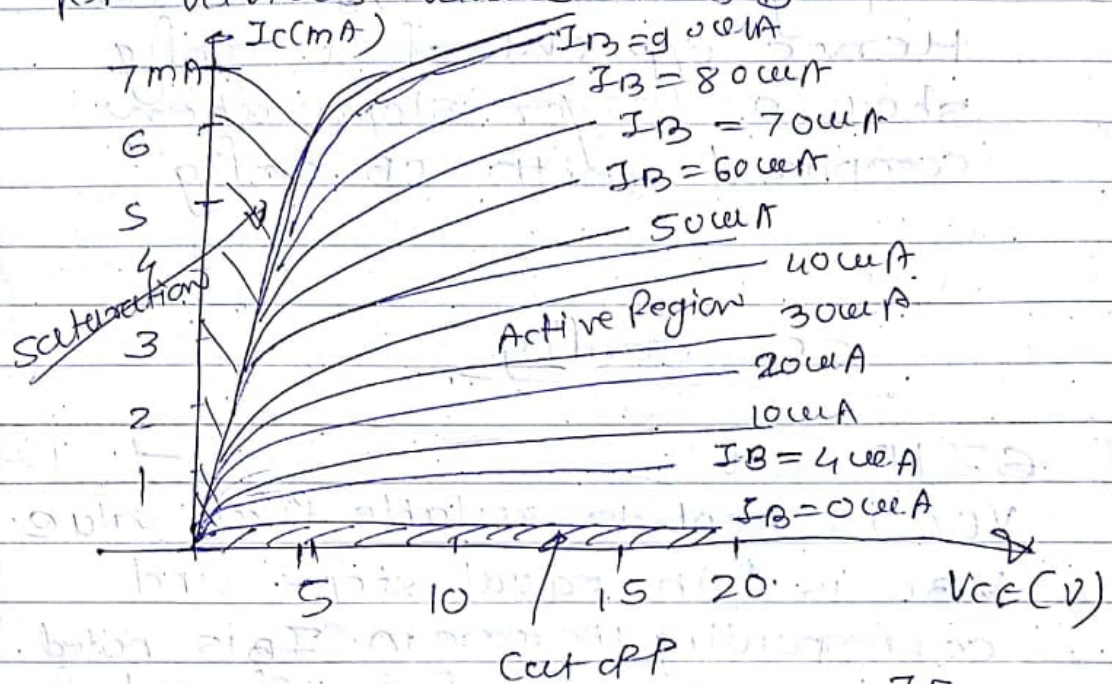
## o/p chrt for cc config

$I_B$  is kept constant by adjusting  $V_{BE}$ .  $V_{CE}$  is increased in suitable equal steps from zero and  $I_C$  is noted for each value of  $V_{CE}$  and plotted for various values of  $I_B$ .



$I_B$  is in  $\mu A$  as compared to  $I_C$  in mA. The curve for  $I_B$  is not horizontal as those obtained for  $I_E$  in CB config indicating collector to emitter voltage will influence the magnitude of collector current.

For larger values of  $V_{CE}$  due to Early effect, a very small change in  $\alpha$  reflected in a very large change in  $\beta$ . For e.g.  $\alpha = 0.98$

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.98}{1-0.98} = 49$$



If  $\alpha$  increases to 0.985 then

$$\beta = \frac{0.985}{1 - 0.985} = 66$$

Here slight increase in  $\alpha$  by about 0.5% results in an increase in  $\beta$  by about 34%. Hence o/p ch of CE config show a larger slope when compared with CB config.


### CC config

EJIP ch

$V_{EC}$  is kept to suitable fixed value.

$V_{BC}$  is  $\uparrow$  in equal steps and corresponding increase in  $I_B$  is noted.

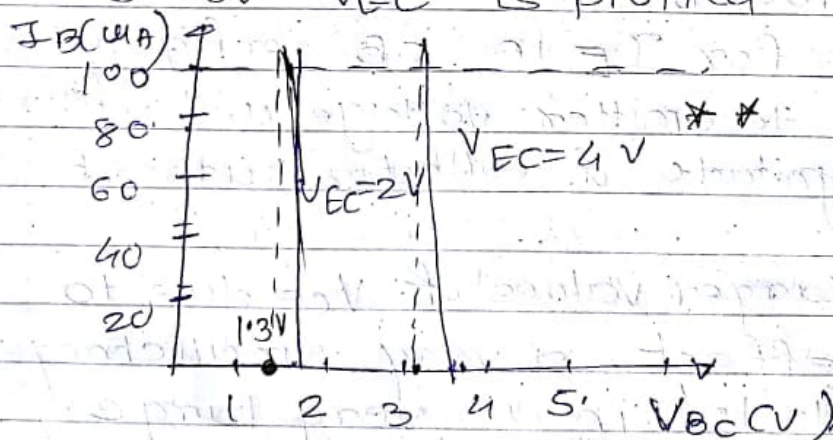
This is repeated for different fixed values of  $V_{EC}$ . Plots of  $V_{BC}$  versus  $I_B$  for different  $V_{EC}$  is plotted.



\*\*\* CC config is known as emitter follower. o/p is taken across emitter. Since voltage gain is unity, we get same o/p as that of IP. Hence we can say that emitter follows IP hence called emitter follower.
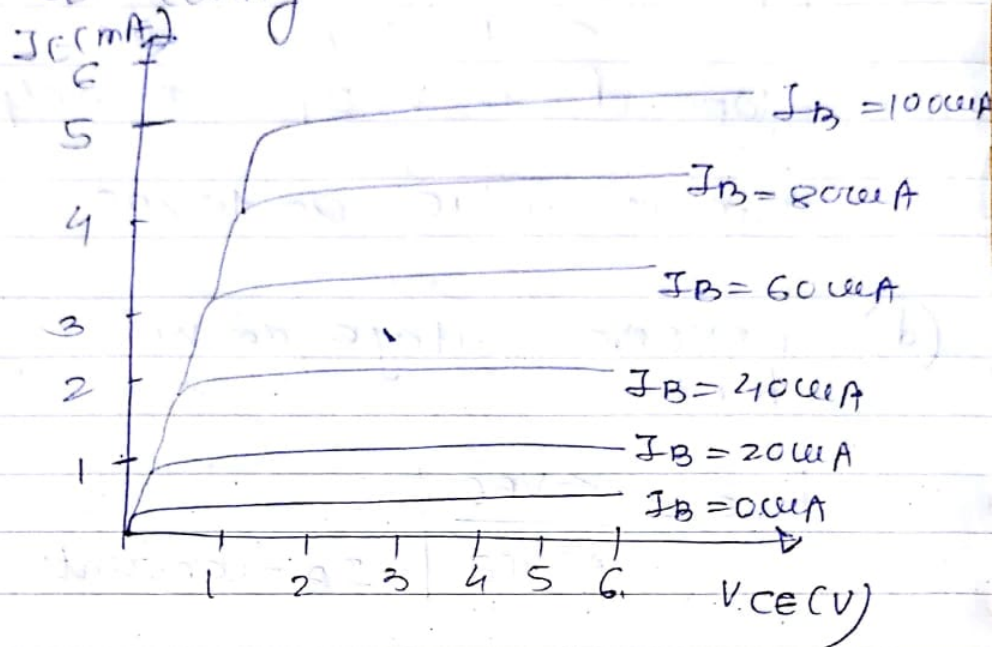
## O/P chrt

O/P chrs of cc are same as that of CE config.



## CE config

$I_{IP}$   $I_{mp}$

$$(a) h_{ie} = \frac{\Delta V_{BE}}{\Delta I_B} \bigg|_{V_{CE} = \text{constant}}$$

slope of  $I_B$  vs  $V_{BE}$  for  $I_{IP}$  chrt

Typical value 500 to 2000  $\Omega$

(b) output admittance  $h_{oe}$

$$h_{oe} = \frac{\Delta I_C}{\Delta V_{CE}} \bigg|_{I_B = \text{constant}}$$

slope of  $I_C$  vs  $V_{CE}$  for  $O/P$  chrt

Typical value 0.1 to 10  $\mu$  ohms



(c) Forward current gain ( $h_{fe}$ ).

$$h_{fe} = \frac{\Delta I_c}{\Delta I_B} \bigg|_{V_{ce} \text{ constant}}$$

slope of  $I_c$  vs  $I_B$  from o/p

Typical value 20 to 200.

(d) Reverse voltage gain.  
 $h_{re}$

$$h_{re} = \frac{\Delta V_{BE}}{\Delta V_{CE}} \bigg|_{I_B = \text{constant}}$$

slope of  $V_{BE}$  vs  $V_{CE}$  from i/p ch.  
Typical value is  $10^5$  to  $10^4$ .

\* \* The CC HP ch is quite different  
from either CB or CC ch.  
The difference is due to the fact that HP  
voltage ( $V_{BC}$ ) is largely determined by  
o/p voltage ( $V_{EC}$ )

$$V_{EC} = V_{EB} + V_{BC}$$

$$\text{or } V_{EB} = V_{EC} - V_{BC}$$

increasing the level of  $V_{BC}$  with  $V_{EC}$  held  
constant and thus reduces  $I_B$  hence.

ch is not almost vertical slightly slope  
around.

(  $V_{EC} = 2 - 1.3V = 0.7$  and BE goes  
in forward bias. For less than 1.3V  
above 1.3V BE less forward bias so  $I_B \downarrow$  )

$$\text{If } 3.3V \text{ } V_{BC}, \quad 4 - 3.3 = 0.7$$